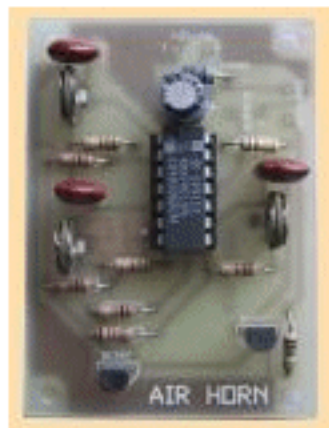


AIR HORN

This kit is available from
Talking Electronics
email Colin Mitchell:
talking@tpg.com.au
for prices and postage



AIR HORN

Add a little extra life to the shunting yard with this dual or triple Air Horn.

One effect rarely included in a model railway is SOUND. Many modellers keep electronics to a minimum so, due to the complexity of the circuits needed to produce sound effects, they are quite often out of the question.

Undoubtedly there are many ways of producing sound effects, ranging from playing recordings of real trains, to complicated circuits which are synchronised to the motion of the trains on the layout.

There are some sound effect chips on the market, but they are not readily available and will not be considered in this book.

The circuit presented here simulates a dual or triple AIR-HORN as used on diesel and electric locomotives. It is based on the versatile CMOS Schmitt Inverter, the 74c14 or CD 40106.

The collector of this transistor is connected to the output of the fourth Schmitt inverter, which is normally LOW, held there by a 100k pull-up resistor on its input.

The emitter of the transistor is held LOW by a 10k pull-down resistor and from the junction of these two components the signal is taken to the output transistor via a 4k7 separating resistor.


When the push button at the enable input is closed, the output of the Schmitt Inverter will go HIGH, taking the collector of the transistor HIGH. The transistor will now function as an emitter-follower. Any signal at its base will appear at its emitter. The signal will be amplified by the second transistor to produce the sound.

When the switch is released, the output of the inverter falls LOW, taking the collector of the transistor LOW.

With the collector LOW, the emitter follower is disabled and no signal can pass to the amplifying transistor and the horn is silent. Why such a complex method of switching?

Wouldn't it be easier to have the push switch wired directly between the oscillators and the amplifier? Or wired so that it switches power to the whole unit?

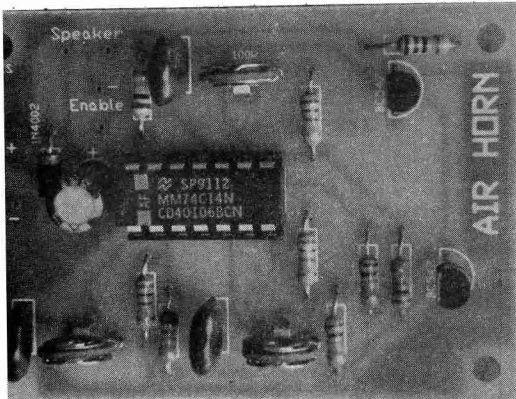This method of switching was chosen because it can be controlled by a digital circuit. An active LOW signal at the enable will sound the horn, which opens great possibilities for automatic control of the horn.




HOW IT WORKS

Only 4 of the six Schmitt Inverters are used in this project, three as oscillators, and the fourth in the gating or control circuit.


Each oscillator consists of a Schmitt Inverter, a 47nF capacitor, a 1k resistor and a 100k mini trim pot. It functions as described in the article on the WARNING LAMP FLASHING UNIT. The only notable differences are that the oscillators in the AIR-HORN project operate at audio frequency and can be adjusted via the trim pot.

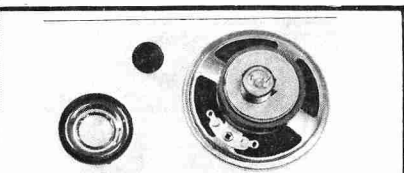
The output of each oscillator is mixed, via a 10k resistor, into the base of a BC 547 transistor which is part of the gating circuit that enables or disables the sound output.



For those who wish to experiment with sound through rails systems, there are several small speakers available. The picture above shows two 12mm Mini-speakers and a 27mm speaker with a standard 58mm or 2 1/4" speaker.

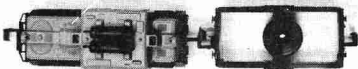The photograph below shows the 12mm speaker inside an 'N' gauge wagon.



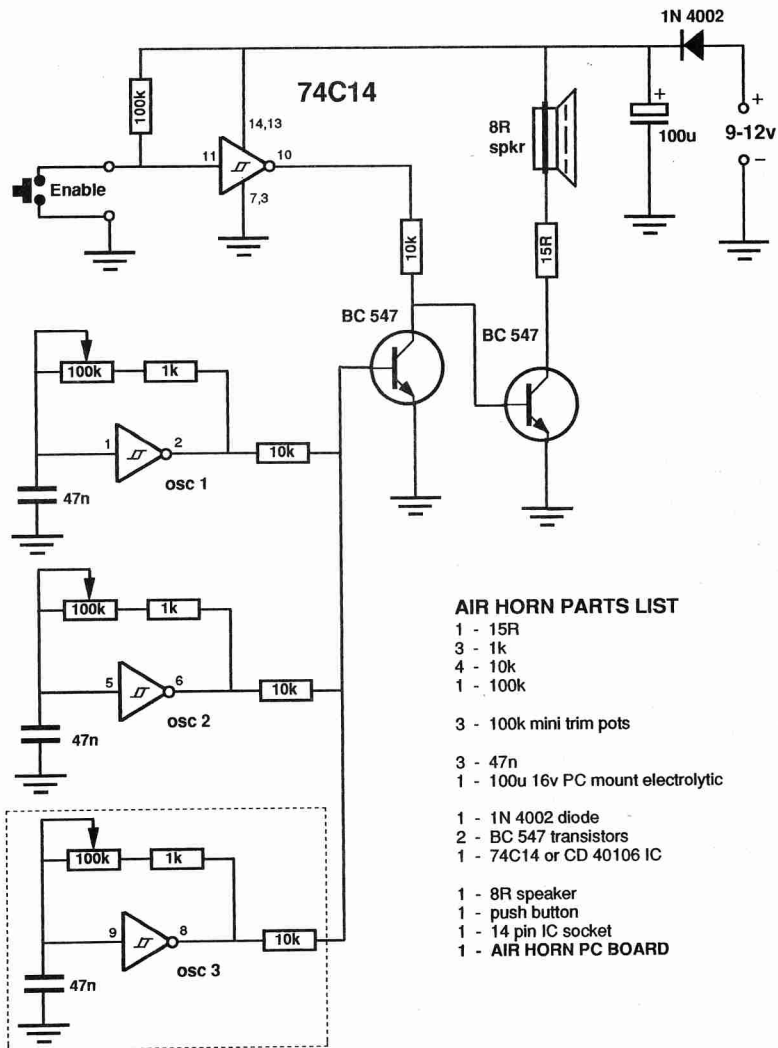

The sections of the Air Horn circuit can be easily seen from this diagram. Oscillator 3, which is drawn inside the dotted box, is omitted for the dual version.

