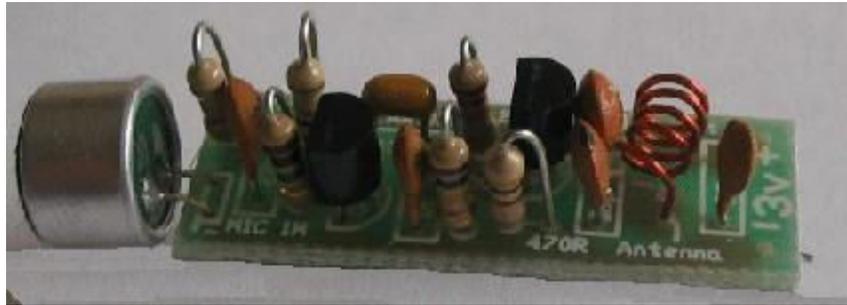



# EARWIG

This kit is designed and manufactured by [TALKING ELECTRONICS](http://TALKING ELECTRONICS)  
For the latest price see: [talkingelectronics.com](http://talkingelectronics.com)



The Complete EARWIG

## A bug in a matchbox . . .

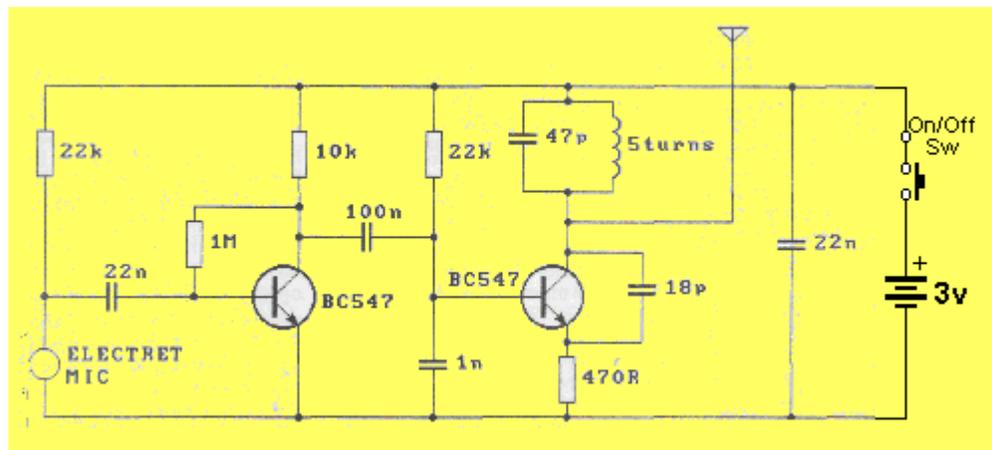

Earwig Circuit

This is an easy to build FM transmitter that fits into a matchbox. It transmits to any standard FM radio and can be used around the home as a baby minder or outdoors for up to 300 metres. Its sensitivity and clarity are very impressive -even the ticking of a clock can be picked up 3 metres away.

Almost everyone has the ambition to use the airwaves. Whether it be for remote control or transmitting halfway around the world, we all love to broadcast.

This project will get you on the air with the least fuss and you can build two units to achieve a two-way link over a range of 300 metres or so.

We've called the project EARWIG because an earwig is a small bug and so is this.

The concept of FM transmission is superb. It produces an extremely high quality signal that is noise-free and it is relatively easy to get a good range with low power.

The Earwig produces no more than 8-10 milliwatts of radiated signal and yet the range is quite impressive.

Buildings and high-voltage transmission lines have an effect on the range and they can sometimes limit the signal to less than 100 metres. But this will be very rare as the signal finds its way through and around obstructions with very little trouble.

The most challenging part of this project is to achieve the best range using 1/2 wave antenna and 3v supply.

By constructing the Earwig, you will learn a lot about FM transmission and see how effective it is. The first question you may ask is: "How can I increase the range?" The answer is not as simple as it seems. A lot of complications creep in when the voltage and power are increased and we must warn you that serious interference may occur to TV sets when you start increasing the supply voltage.

Everything is quite safe when you are down at 10 milliwatts and although you can achieve 300 metres, the signal strength at this distance is only a few microvolts and you are almost down to snow.

These FM transmitter projects are for interest and educational purposes only and have a magnetic draw about them.

You can spend hundreds of hours experimenting and improving the design and sometimes you come right back to square one.

We have done all the experimenting for you and come up with the simplest and best design. It is small enough to fit inside a match box and comes with a 15cm antenna for inter-room communication.

We have had a unit running for nearly 12 months. It sits on top of the TV during news and similar programs and the writer has an FM radio next to his typewriter. He can monitor the TV while typing and if an important item comes up, he can rush in and watch it.

Mind you, most programs need very little viewing and when the adverts come on, you can turn the radio down for up to 2 minutes. It's amazing what can be done in two minutes!

The Earwig can also be used as a baby monitor for those times when you are next door or in the garden.

It's left in the children's bedroom and if they wake up and start crying, you can attend to them quickly.

The unit looks a bit like a video sender and you can use any one of a number of boxes to house the circuit: or, as we have suggested, you can use the humble matchbox.

The current consumption is less than 5 milliamps and you should get between 80 and 100 hours of operation on two 'N' cells.

The circuit has been designed for maximum output rather than immunity to stray capacitance and although it has a very low drift factor, it is not possible to touch the circuit without it drifting off frequency. A 'tight' circuit will be described in another project as the output has to be kept to a minimum if the frequency is to be stable when the circuit is handled.

Although the circuit is not crystal locked, the frequency drifts very little in normal operation and our tests showed a receiver did not need re-tuning after an 8 hour test. The only thing that will influence the output frequency is the condition of the batteries. As they age, the frequency changes slightly.

A reduction in the transmitting range will indicate the voltage has fallen to the minimum allowed and the cells should be replaced. They are soldered together to fit inside the matchbox and provided they are soldered quickly, the seal on top of each cell will not be damaged and they will not leak.

All the components are easy to obtain and if you know what you are doing, you can use parts from your own sources. If you have any hesitation about wire size, coil diameter, identifying a monoblock capacitor, reading 10p or 1n on a ceramic or the type of electret microphone to use, you should buy a kit.

Kits are available from Talking Electronics as are ALL our projects, and the complete kit of parts includes a pre-wound coil and PC board with an overlay. The only item you need to buy is a matchbox and perhaps a few fake matches.

## HOW IT WORKS

The circuit consists of two stages, an audio amplifier and an RF oscillator.

The electret microphone contains a FET transistor and you can count this as a stage if you wish. The FET amplifies the change in capacitance of the diaphragm at the front of the microphone and this is why electret microphones are so sensitive.

The first transistor is the audio amplifier stage and has a gain of 20 to 50 and amplifies the signal for injection into the base of the RF oscillator stage.

This stage is designed to operate at 88MHz and the frequency is set by the inductance of the 5-turn coil, together with the 47pF capacitor. The frequency is also determined by the transistor, the 18pF feedback capacitor and also to a lesser extent by the biasing components.

When power is applied, the 1nF base capacitor will gradually charge via the 22k resistor. But the 18pF will charge much faster, via the oscillator coil and the 470R resistor. The 47pF will also charge (although only a very small voltage will appear across it) and the coil will produce a magnetic flux. As the base voltage gradually rises, the transistor will turn ON and effectively put a resistance across the 18pF,

A few difficult-to-describe cycles will now occur while the 1nF charges to the operating voltage of the stage and we will resume our discussion when this is nearly reached.

The base voltage will continue to rise and the 18pF will have the effect of trying to prevent the emitter from moving. A point in time is reached when the energy from the capacitor is exhausted and it can no longer resist the movement of the emitter. The base-emitter voltage decreases and turns the transistor off. The current flow in the coil then ceases and the magnetic flux collapses.

This collapsing magnetic field produces a voltage in the opposite direction and whereas the collector voltage may have been 2.9V, it will now rise to over 3V and charge the 47pF in the opposite direction. This voltage will have the effect of charging the 18pF and the voltage drop across the 470R emitter resistor will be such that the transistor will be turned more firmly OFF.

As the 18pF charges, the emitter voltage will drop to a point where the transistor will begin to turn ON and the current flow through the coil will oppose the collapsing magnetic field.

The voltage across the coil will reverse and the collector voltage will drop. This change will be passed on to the emitter via the 18pF and the result will be that the transistor will turn ON very hard and short out the 18pF. After this the cycle begins again.

What we have is an oscillator circuit that produces AC energy at 88MHz with the amplified audio signal fed into this stage via the 100nF varying the frequency of oscillation to produce the FM signals.

## CONSTRUCTION

Before commencing construction it's a good idea to place the two cells and PC board into the matchbox and see how much room you have. The headroom is most critical as you need to leave space for a single row of matches on a thin sheet of card. In fact you can glue a few dead matches on the card to add more reality.

Lay all the components on the work bench and identify each of them. There's nothing more annoying than putting two components on the board incorrectly and having to change them later. To avoid this, place the parts so that they match the positions on the board. This will allow you to concentrate on soldering.

The solder we recommend is superfine .71mm resin core type, as thin solder makes a much neater connection. As one salesman told us "It goes twice as far!"

A small 15 to 20 watt iron is needed and provided the tip is cleaned on a wet sponge before starting, you will have no trouble in producing a first class job.

The only item that needs fabricating is the coil. It can be wound with .5mm or .71mm enamelled or tinned copper wire.




Although the wire diameter is important, it is not as critical as the number of turns, the diameter of the coil or its length.

Wind 5 turns on a 3mm diameter shaft such as a medium Philips screwdriver and space the turns

as shown in the photos, over about 5.5mm.

Final setting of the frequency will be done by stretching the turns apart or squashing them together and at this stage the coil is ready for fitting. If you have made the coil from enamelled wire, the ends should be tinned up to the point where they enter the PC board. This tinning is done while the coil is on the screwdriver to act as a heatsink and any surplus solder should be removed so that the ends will fit down the holes in the board.

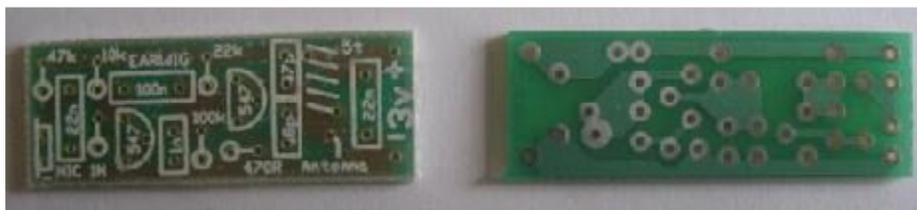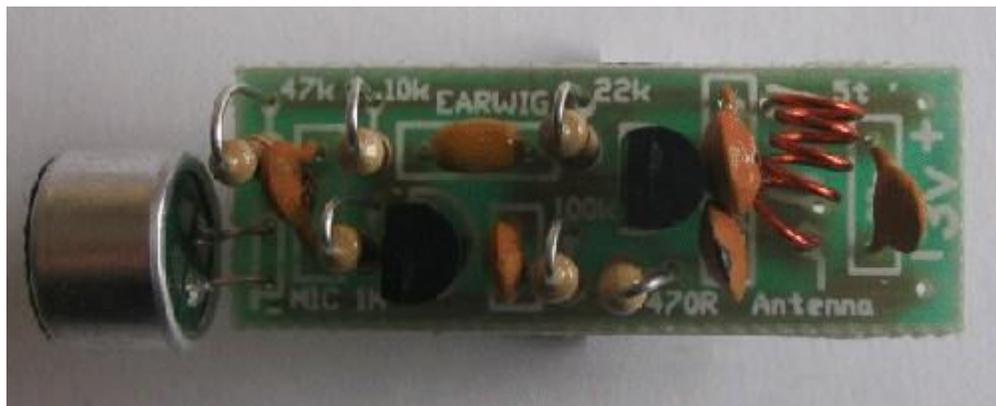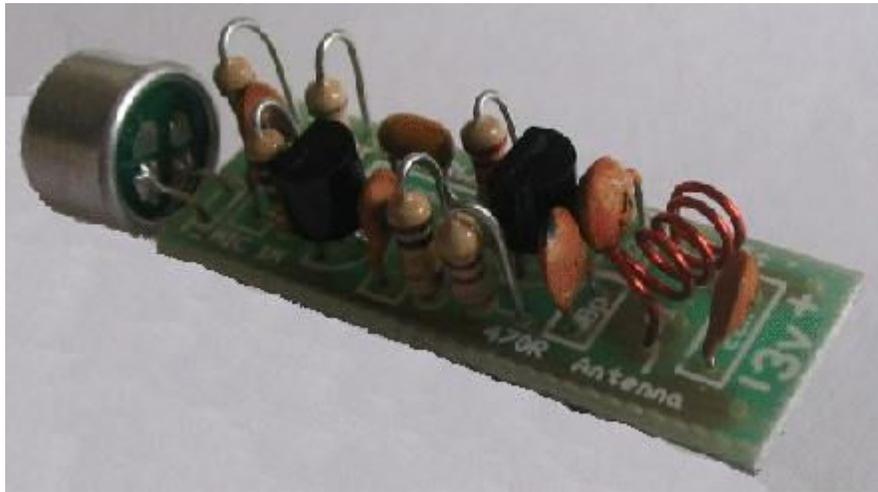Now you can wire up the PCB (printed circuit board). Start at the microphone end of the board but leave the microphone to last to prevent the leads being damaged when fitting the rest of the parts.



**Top and underside of the EARWIG PC board**

The resistors stand on end and fit firmly up to the board, to keep the height to a minimum. Continue across the board, fitting each part as you come to it. The transistors should be pushed down so that they are only as high as the other components. Add everything, including the microphone and finally the batteries, switch and antenna.

The batteries are soldered together by using the switch and some tinned copper wire at one end and soldered to the board with a short length of tinned copper wire from the positive terminal and hook-up wire from the negative terminal.

Solder 15cm of tinned copper wire to the point marked "Antenna" on the board and construction is complete.

## WHY?

Have you ever wondered why a circuit doesn't work? How many times have you built a project from a magazine and it doesn't function as described?

Don't blame yourself or blame the magazine. Most of the time it's due to a factor called tolerance. As made by the manufacturer, all components have a value falling inside a "spread range" rather than the nominal value marked on them. The width of this range is known as the tolerance. So if the tolerance is said to be 5%, it means the value of a particular part will be anywhere between 5% below and 5% above its marked value.

Tolerance applies to resistors, capacitors, transistors, microphones, coils integrated circuits and almost anything you can think of.

Then we have another factor called limits. For each component in a circuit there will be a range of allowable values for that part. Providing the value remains inside that range, or inside the limit, the circuit will work properly. Normally each components value is chosen so that it falls inside this range.

Most circuits are not very critical and for any particular component they will generally work equally well if we select the next higher or lower value. If not, the circuit is either very critical or the chosen value is the most appropriate.

When you place a circuit on the open market, such as in a magazine, you have an enormous range of potential builders, drawing their supplies from many different sources. Sometimes they use the designated values and sometimes they select the next value. Also some components have a close tolerance while others have a wide tolerance, such as +/- 50%. When the spreads and limits are combined in a random manner, you can quite often end up with a circuit that doesn't work!

Take the electret microphone for example. On a 3v supply, some microphones are super-sensitive with a 100k load resistor. Others may require 4k7 to get a barely acceptable sensitivity. You can not tell the two apart from the outside. They both look the same. But electronically they are quite different.

We are talking here of hundreds of percent difference, whereas the manufacturer's specifications state one has a sensitivity of -22dB and the other -54dB. In simple terms we can say every 3dB down is twice the sensitivity, making the -54dB unit about 2,000 times more sensitive!

The same can apply to transistors. The specification sheets may show two devices to be nearly the same and yet when they are connected to a circuit, one will work perfectly while the other will fail to operate.

This is one of the reasons why the kit market has flourished. Kits are generally put together from batches of parts that have been tried in the circuit and for this reason we are advocating first-time constructors invest in a kit.

You have the greatest potential for success and nothing is more encouraging than success.

## SETTING UP

Once all the components have been soldered in position, the project can be set up and tested for performance. The test procedure is to add a short antenna (about 5 - 15cm long) to the antenna point on the board and tune an FM radio across the band, looking for the signal.

It is best to keep the transmitter some distance from the radio, to prevent any of the harmonics (side tones) from being picked up.

If you cannot detect the carrier, it may mean the frequency is below the band. Move the turns of

the oscillator coil apart a little and try again. If you are using tinned copper wire, make sure none of the turns are touching. If you are using enamelled wire, make sure the coil has continuity by either measuring it with a multimeter set to low ohms or measuring the current taken by the circuit, which should be about 4-6mA.

Once the carrier is detected, you can check the sensitivity of the front end by placing the Earwig near a clock. The ticking should come through loud and clear and the circuit should be more sensitive than your ear.

The load resistor for the electret microphone (22k) will determine the sensitivity and it may have to be lowered to 10k or raised to 47k, depending on the sensitivity required.

Make sure the frequency of transmission is well away from any of your local FM radio stations as a signal from a station will swamp the Earwig when you are testing for range.

By moving the turns of the coil together, the frequency will be lowered and if the turns are spread apart, the frequency will increase. This saves using a tuning capacitor and keeps the cost down but you can use a trimmer if you wish.

A word of assistance here. If you use a 5-65p air trimmer, for example, it will be very difficult to tune the circuit to a

specific frequency as a few pF (picofarads) will change the frequency by 1 MHz or more. It is better to use a 39p ceramic and put a 4-11p trimmer across it. This way you are fine tuning the circuit and you have much more leeway with adjustment.

Theoretically the inductor should also be adjusted to maintain the L/C ratio of the tuned circuit, but over the small range we require, this is not critical.

The output power of the Earwig can be determined by using an FM radio with a tuning indicator. You really need to have a comparison as 4 divisions on the meter of our tuner indicates a very good output. We tested the output of our prototype with a 15cm length of antenna laying horizontally and about 10 metres from the tuner. With 4 divisions we know the transmitter will be capable of transmitting about 300 metres with a half wave (170cm) antenna.

## **IF IT DOESN'T WORK**

Hopefully the Earwig will work first go for you, but if it doesn't, you will have a challenge. An educational challenge.

if you cannot pick up the carrier on an FM receiver you should firstly assume the frequency is below the normal 88-108MHz band.

Measure the current. If it is about 4-6mA, the circuit will be operating. Move the turns of the coil apart and sweep the band with the radio. When touching any of the parts on the board, make sure you use a non-metallic screwdriver and also keep away from the batteries etc.

The capacitance effect of your hand will detune the circuit appreciably and it may drop out completely. It all depends how critical the tolerance values are, in your case. It is also important to keep to the 3v supply and place the batteries close to the board, as shown in the photos. Don't use a plug pack or power supply to derive the voltage as the circuit may not like the characteristics of a generated supply.

The whole layout must be exactly as shown to maintain the same circuit capacitances. Once you get the circuit working, you can change the arrangement but during the initial test procedure, everything must be as shown.

The oscillator is operating at about 88MHz and unless you have a 100MHz CRO, you cannot detect the output waveform. If you are fortunate enough to have a frequency counter, the antenna can be connected directly to the 75 ohm input and the frequency measured.

Otherwise it will be necessary to make some DC voltage readings to see if the oscillator transistor is biased correctly.

Measure the base voltage and also the emitter voltage. An ordinary voltmeter will indicate about 2v in both cases, due to the loading of the meter. Only a high impedance meter such as a FET meter will indicate 2v on the emitter and 2.5v on the base.

If a voltage is present in both cases, you can assume the transistor is operating, but it may be transmitting at the wrong frequency.

The 18p feedback capacitor suits a BC 547 transistor. If you intend to use another type, the value can be decreased to 10p or 5p6. Try changing this capacitor first, then the transistor.

Simple things such as shorts on the PC board, broken tracks, poorly soldered joints or unmarked

components are always a possibility. Especially components with poor markings. If you are unsure about the value of a component, replace it immediately. It could be ten times the correct value, and the circuit will never work!

If you are detecting a carrier but no audio, the fault will lie in the audio stage and/or the microphone. These two sections can be tested with a CRO and you can measure the audio signal to see what is being presented to the oscillator stage.

Without a CRO you will be stuck. Even though the voltage on the electret mic can be as low as 70mV to 1500mV, this will not indicate its sensitivity or if it is working at all.

A voltage of 1.4v on the collector of the audio amplifier will indicate the transistor is turned ON and if it is below .8v, the transistor will be saturated or possibly damaged in some way. It could also mean the transistor has a very high gain and will not be suitable.

If the voltage is above 2.5v, the stage will not be turned ON sufficiently and again, the transistor and bias resistor should be checked and/or replaced.

A CRO will also show the sensitivity of the microphone. By increasing or lowering the value of the load resistor, the gain of the FET can be changed. It should not go below 10k and may need to be as high as 47k, or higher, for extremely sensitive devices.

It works like this: for any electret microphone, reducing the load resistor will increase the sensitivity. The final value will depend on the quality of the microphone.

This is about as far as you can go with simple test equipment. If all fails, start again with a new kit. Sometimes something stupid has occurred such as swapping two components or reading the value of a resistor incorrectly and this will be extremely difficult to find.

## **FITTING INTO A CASE**

All the components can be mounted in the tray of a matchbox and if the PC board is turned on its side, it will take up the least amount of space. It is then covered with a layer of matches. The antenna can be a length of hook-up wire or fine enamelled wire.

Cover the "works" with a single layer of matches, stuck to a thin piece of card and take the antenna out one end of the tray or up through the roof.

A small hole can be made in the other end of the tray to allow the sound to enter the microphone but this is not really necessary as the sound seems to get through, even when the drawer is closed.

If a hole is made in the side of the tray, near the switch, the circuit can be turned on by pushing a match through the hole and this will save removing the layer of matches.

We suggest only a very short length of antenna, about 15cm, to achieve a range of about 30 metres. This will be sufficient for inter-room communication and will be ample for even a large house.

The complete project looks very nice painted black, with the short antenna mounted upright to look like a video amplifier.

I know you will be impressed with its performance. After this, the next model to build is the Amoeba or Voyager and then the Spy Bug.

## **PARTS LIST**

1 - 470R

1 - 10k

2 - 22k

1 - 1M

1 - 18p ceramic

1 - 47p

1 - 1n

2 - 22n

1 - 100n monoblock

2 - BC 547 transistors

1 - electret mic insert

1 - mini slide switch

1 - 5 turn coil 3mm dia tinned copper wire

2 - 'N' cells

1 - 15cm tinned copper wire for short  
antenna

1 - 170cm antenna wire

**1 - EARWIG PC board**

1/10/07